

实验三：LC3 系统-ALU 模块设计

1. 实验目的

- 1.1. 熟悉 LC3 微结构。
- 1.2. 学习设计 ALU 的前置 Chisel 语法。
- 1.3. 掌握 LC3 系统中 ALU 模块的设计。
- 1.4. 掌握使用单元测试验证 LC3 系统中的 ALU 模块。

2. 实验内容


- 2.1. 阅读 《计算机系统概论》 附录 C，了解 LC3 微结构。
- 2.2. 阅读本实验前置 Chisel 语法。
- 2.3. 根据实验指导设计 ALU 模块。
- 2.4. 根据实验指导对 ALU 模块进行单元测试。

3. 实验步骤

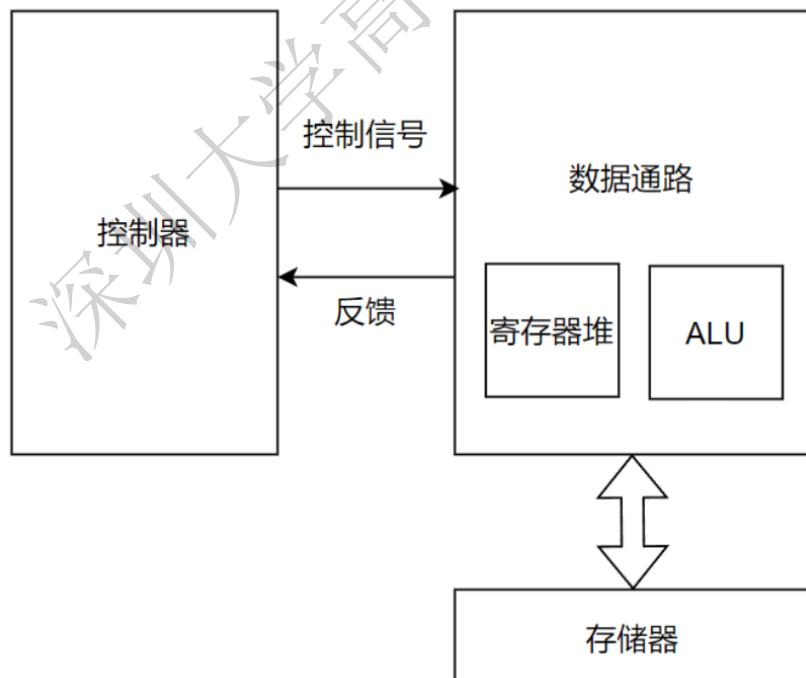3.1. 学习 LC3 结构

《计算机系统概论》 附录 C 中的内容为 LC3 内部架构的细节和规范，相当于设计的图纸，熟悉内部架构对后续实验有极大帮助。

在完成前两章实验，相信大家对基本的硬件设计概念与 Chisel 语言有所了解，实验三至七将会根据模块自第向上完成 LC3 的设计。在整体实验前我们需要熟悉 LC3 的整体架构，从模块上看 LC3 主要分为三个大模块，即控制器、数据通路和存储器，其中数据通路中包含两个较为重要的模块，ALU 和寄存器堆，结构如下图所示。



三个大模块的工作流程为控制器发送控制信号到数据通路，数据通路根据信号进行取指、运算、访存等操作，其中访存操作数据通路会读写存储器。完成操作后数据通路将一些结果信号返回给控制器，控制器依据结果转换内部状态机，

生成新的控制信号，并重复“控制器发送控制信号——数据通路进行操作并返回结果——根据结果发送新控制信号”的流程。

根据以上架构，按照模块设计将分为五个实验，内容如下：

- 实验三：实现 LC3 的 ALU 模块，并对其进行单元测试。
- 实验四：实现 LC3 的寄存器堆模块，并对其进行单元测试。
- 实验五：实现 LC3 的控制器堆模块，并对其进行单元测试。
- 实验六：实现数据通路中的关键电路的设计。
- 实验七：了解 LC3 存储器的设计。

重要勘误

注意：如果你使用的是虚拟机，后续实验的代码放置在 `~/Frontend/chisel_lc3` 文件夹中

实验开始前，请在 `chisel_lc3` 文件夹的 `scala` 文件全部添加上一个 `.bak` 的后缀，否则使用 `mill` 运行仿真的时候会有各种报错，这是因为实验代码将部分内容留空给学生进行填空，这会导致 `mill` 的编译提示语法错误，如下图所示：

```
lc3@lc3-virtual-machine:~/Frontend/chisel_lc3$ mill chisel_lc3.test.testOnly example.WireTest
[37/71] chisel_lc3.compile
[info] compiling 9 Scala sources to /home/lc3/Frontend/chisel_lc3/out/chisel_lc3/compile.dest/classes ...
[error] /home/lc3/Frontend/chisel_lc3/src/main/scala/LC3/DataPath.scala:150:3: illegal start of simple expression
[error]   val dstData = WireInit(regfile.io.wData)
[error]   ^
[error] one error found
1 targets failed
chisel_lc3.compile Compilation failed
```

统一添加后缀的命令方式如下：

```
cd src
```

```
find . -name "*.scala" -exec bash -c 'mv "$0" "${0}.bak"' {} \;
```

如果你想全部去除这个后缀，命令如下：

```
cd src
```

```
find . -name "*.scala.bak" -exec bash -c 'mv "$0" "${0%.bak}"' {} \;
```

添加后缀之后，需要根据实验使用到的文件将文件的 `.bak` 后缀去掉，例如下面的实验中使用到了 `src/test/scala/example/Wire.scala` 这个文件，此时已经被重命名为了 `src/test/scala/example/Wire.scala.bak`，那么我们需要将其重新命名回来：

```
mv src/test/scala/example/Wire.scala.bak src/test/scala/example/Wire.scala
```

接下来就能正常使用了：

```
mill chisel_lc3.test.testOnly example.WireTest
```

在接下来的实验中，你都需要执行类似的操作来将一些需要使用到的文件的 `.bak` 后缀移除，并且如果 `mill` 命令已经能正常执行就不需要将这个后缀添加回去！


在接下来的实验中，你都需要执行类似的操作来将一些需要使用到的文件的 `.bak` 后缀移除，并且如果 `mill` 命令已经能正常执行就不需要将这个后缀添加回去！

在接下来的实验中，你都需要执行类似的操作来将一些需要使用到的文件的 `.bak` 后缀移除，并且如果 `mill` 命令已经能正常执行就不需要将这个后缀添加回去！

3.2. Chisel 语法学习

 (1) Wire

电路中最基本的组件就是线，在 Chisel 中定义为 Wire。下图展示了一个只有一条线的模块，该模块只有一个输入端口 in，一个输出端口 out，in 端口信号直接通过线连接到 out。



在 Chisel 中一个线的定义为 `val aWire = Wire(UInt(1.W))`，其中 `aWire` 是线的名称，`Wire` 表示这是一个线类型，`UInt` 表示用整数表述信号，`1.W` 表示该线宽度为 1 比特。

完成线的定义，还需要把线连接起来，在 chisel 中连线操作符为 `:=`，如上图若定义绿色线为 `aWire`，则其连线为 `aWire := io.in` 和 `io.out := aWire`。当然，也可以直接 `io.out := io.in`，其结果是一样的。

下列代码 (`src/test/scala/example/Wire.scala`) 定义了上图模块和简单测试：

```
// 示例Wire模块
class Wire extends Module {
  val io = IO(new Bundle {
    val in  = Input(UInt(1.W))
    val out = Output(UInt(1.W))
  })

  val aWire = Wire(UInt(1.W)) // 线定义

  aWire := io.in              // 线连接
  io.out := aWire
}

// 示例测试
class WireTest extends AnyFlatSpec with ChiselScalatestTester {

  it should "test wire" in {
    test(new Wire) { c =>
      c.io.in.poke(0.U)
      println(s"输入: ${c.io.in.peek}, 输出: ${c.io.out.peek}")

      c.io.in.poke(1.U)
      println(s"输入: ${c.io.in.peek}, 输出: ${c.io.out.peek}")
    }
  }
}
```

可以在项目根目录键入 `mill chisel_lc3.test.testOnly example.WireTest` 命令进行测试，其结果如下，输入信号为 0 时，输出也为 0，输入为 1 时输出也为 1。

```
$ mill chisel_lc3.test.testOnly example.WireTest
[71/71] chisel_lc3.test.testOnly
WireTest:
输入: UInt<1>(0), 输出: UInt<1>(0)
输入: UInt<1>(1), 输出: UInt<1>(1)
- should test switch
```

(2) 简单逻辑操作符

电路中常用的运算有与、或、非、异或、加法等，运算符分别为 $&$ $|$ \sim \wedge $+$ 具体测试代码（src/test/scala/example/Logic.scala）如下：

```
// 示例Logic模块
class Logic extends Module {
  val io = IO(new Bundle {
    val ina = Input(UInt(2.W)) // 示例测试
    val inb = Input(UInt(2.W))
    val add = Output(UInt(2.W))
    val and = Output(UInt(2.W))
    val or = Output(UInt(2.W))
    val not = Output(UInt(2.W))
    val xor = Output(UInt(2.W))
  })

  io.add := io.ina + io.inb
  io.and := io.ina & io.inb
  io.or := io.ina | io.inb
  io.not := ~io.ina
  io.xor := io.ina ^ io.inb
}

// 示例测试
class LogicTest extends AnyFlatSpec with ChiselScalatestTester {

  it should "test logic" in {
    test(new Logic) { c =>
      c.io.ina.poke("b01".U)
      c.io.ina.poke("b10".U)
      println(s"输入ina: ${c.io.ina.peek}, 输入inb: ${c.io.inb.peek}")
      println(s"输出add: ${c.io.add.peek}")
      println(s"输出and: ${c.io.and.peek}")
      println(s"输出or : ${c.io.or.peek}")
      println(s"输出not: ${c.io.not.peek}")
      println(s"输出xor: ${c.io.xor.peek}")
    }
  }
}
```

模块有两个输入端口，五个输出端口，均为 2bits。五个输出端口分别对输入端口做加、与、或、非、异或操作。测试模块对 ina 端口输入 01，对 inb 端口输入 10，检测五个输出端口数值。

键入测试命令得到结果：mill chisel_lc3.test.testOnly example.WireTest

```
LogicTest:
输入ina: UInt<2>(2), 输入inb: UInt<2>(0)
输出add: UInt<2>(2)
输出and: UInt<2>(0)
输出or : UInt<2>(2)
输出not: UInt<2>(1)
输出xor: UInt<2>(2)
- should test logic
```

(3) Switch

除了基本的与或非逻辑，在电路中还有一种选择逻辑，在 Chisel 中常用 Mux、When、Switch 来生成选择逻辑，本段介绍 Switch，具体语法为：

```
Switch(pattern) {
  is(match1) { logic1 }
  is(match2) { logic2 }
  ...
}
```

当 pattern 符合 match1 时，就会选择生成 logic1，当 pattern 符合 match2 时会选择生成 logic2。

示例代码（src/test/scala/example/Switch.scala）模块如下：

```
// 示例Switch模块
class Switch extends Module {
  val io = IO(new Bundle {
    val ina    = Input(UInt(4.W))
    val inb    = Input(UInt(4.W))
    val select  = Input(UInt(1.W))
    val result  = Output(UInt(4.W))
  })

  io.result := 0.U

  switch (io.select) {
    is(0.U) {io.result := io.ina}
    is(1.U) {io.result := io.inb}
  }
}

// 示例测试
class SwitchTest extends AnyFlatSpec
  with ChiselScalatestTester {

  it should "test switch" in {
    test(new Switch) { c =>
      c.io.ina.poke(3.U)
      c.io.inb.poke(6.U)
      c.io.select.poke(0.U)
      println(s"select为${c.io.select.peek}, " +
              s"result为${c.io.result.peek}")

      c.io.select.poke(1.U)
      println(s"select为${c.io.select.peek}, " +
              s"result为${c.io.result.peek}")
    }
  }
}
```


输入两个四位数据，一个一位选择信号，输出一个四位数据。该模块使用 Switch 实现选择功能，当 select 信号为 0 时，result 选择 ina 信号，否则选 inb 信号。在测试中 ina 输入 3.U, inb 输入 6.U, select 分别输入 0.U 和 1.U 观察 result 结果。

键入 `mill chisel_lc3.test.testOnly example.WireTest` 得到测试结果如下：

```
[71/71] chisel_lc3.test.testOnly
SwitchTest:
select为UInt<1>(0), result为UInt<4>(3)
select为UInt<1>(1), result为UInt<4>(6)
- should test switch
```

以上介绍了部分组合电路的语法，更多语法简介见文末附录 Chisel Cheat Sheet。

3.3. ALU 模块的设计

 

LC3 ALU 模块中需要接收三个输入，即操作数 1，操作数 2，和操作类型，并且得到一个输出。LC3 ALU 中支持的运算操作共四类，加法、按位或、按位反以及取操作数 1。在 ALU 运算时会根据上述的输入类型进行选择做何种运算（2bits 的操作类型可表示四种操作），其中操作类型的 2bits 来自于控制器的 SIG_ALUK 信号。因此其模块端口和操作类型如下表所示：

端口名称	方向	位宽	操作类型	功能
操作数1	输入	16 bits	SIG_ALUK = 0	加法
操作数2	输入	16 bits	SIG_ALUK = 1	按位与
操作类型	输入	2 bits	SIG_ALUK = 2	对操作数1取反
输出数据	输出	16 bits	SIG_ALUK = 3	取操作数1

在有了上述端口和功能描述后，将其用 Chisel 代码描述。

(src/main/scala/LC3/ALU.scala)

```
class ALU extends Module{
  val io = IO(new Bundle{
    val ina = Input(UInt(16.W))
    val inb = Input(UInt(16.W))
    val op  = Input(UInt(2.W))    //ADD,AND,NOT,PASSA
    val out = Output(UInt(16.W))
  })


  io.out := DontCare

  // 实验三 任务一
  // 在此编写ALU逻辑
}
```


实验三-任务一：在 ALU.scala 文件中编写 ALU 逻辑（提示，可使用上述介绍语法描述该电路）

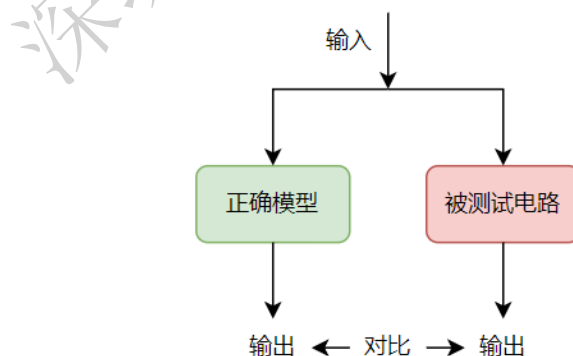3.4. ALU 模块的单元测试

完成设计之后，我们需要对 ALU 的功能进行验证。除了在第三章中使用简单的结果观察方法（容易出错），在数字电路中的验证方法通常采用一个正确的模型（golden modle）去和我们的设计进行对比。给正确模型和被测试的电路给同样的输入，判断输出是否正确。



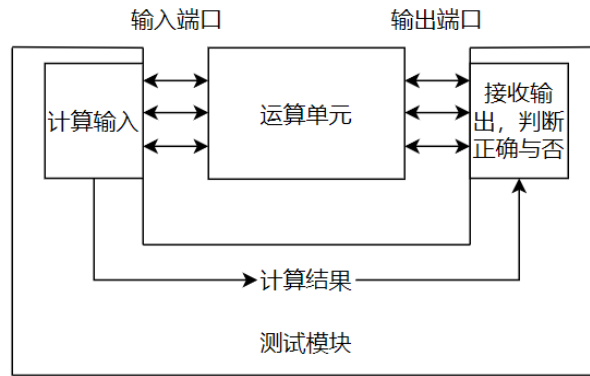在 chisel 设计中最容易获得的模型便是使用 scala 编写的，从另一个角度看第三章单元测试的原理图，其结构大致相同，只是模块的输入输出不再是自己定义而是由程序自己计算好。原理如下图所示。



ALU 测试代码 (src/test/scala/ALUTest.scala) 如下, 其中本测试用例给出 golden module 的生成和 add 的功能测试, 输入如下命令对 ALU 进行仿真验证。

```
mill chisel_lc3.test.testOnly LC3.ALUTest
```

```
class ALUTest extends AnyFlatSpec with ChiselScalatestTester {

  def TEST_SIZE = 10

  val ina, inb, add_out, and_out, not_out, pass_out = Array.fill(TEST_SIZE)(0)

  // 生成正确模型结果
  for (i <- 0 until TEST_SIZE) {
    ina(i) = Random.nextInt(0xffff)
    inb(i) = Random.nextInt(0xffff)
    add_out(i) = ina(i) + inb(i)
    and_out(i) = ina(i) & inb(i)
    not_out(i) = 0xffff - ina(i)
    pass_out(i) = ina(i)
  }

  // 硬件部分
  it should "test add" in {
    test(new ALU) { c =>
      for (i <- 0 until TEST_SIZE) {
        c.io.ina.poke(ina(i).U)
        c.io.inb.poke(inb(i).U)
        c.io.out.expect(add_out(i).U(15,0))
        println(s"${i}. ina=${ina(i)} inb=${inb(i)}")
        println(s"${i}. 标准结果 add_out=${add_out(i) % (1<<16)} 模块结果 io.out=${c.io.out.peak}")
      }
    }
  }
}
```

输出结果为:

```
ALUTest:
0. ina=29156 inb=58051
0. 标准结果 add_out=21671 模块结果 io.out=UInt<16>(21671)
1. ina=17457 inb=50141
1. 标准结果 add_out=2062 模块结果 io.out=UInt<16>(2062)
2. ina=59201 inb=34146
2. 标准结果 add_out=27811 模块结果 io.out=UInt<16>(27811)
3. ina=33054 inb=2740
3. 标准结果 add_out=35794 模块结果 io.out=UInt<16>(35794)
4. ina=36058 inb=58677
4. 标准结果 add_out=29199 模块结果 io.out=UInt<16>(29199)
5. ina=734 inb=420
5. 标准结果 add_out=1154 模块结果 io.out=UInt<16>(1154)
6. ina=55545 inb=40688
6. 标准结果 add_out=30697 模块结果 io.out=UInt<16>(30697)
7. ina=53167 inb=2985
7. 标准结果 add_out=56152 模块结果 io.out=UInt<16>(56152)
8. ina=64668 inb=19943
8. 标准结果 add_out=19075 模块结果 io.out=UInt<16>(19075)
9. ina=49390 inb=31438
9. 标准结果 add_out=15292 模块结果 io.out=UInt<16>(15292)
- should test add
```

实验三-任务二：模仿上述 add 测试用例，在 ALUTest.scala 文件中编写 and, not, pass 功能的测试用例。

附录:

Chisel3 Cheat Sheet

Version 0.5.3 (beta): January 17, 2022

Notation in This Document:
For Functions and Constructors:
Arguments given as `kwd:type` (name and type(s))
Arguments in brackets (`[...]`) are optional.
For Operators:
`c, x, y` are Chisel Data; `n, m` are Scala `Int`
`w(x), w(y)` are the widths of `x, y` (respectively)
`minVal(x), maxVal(x)` are the minimum or maximum possible values of `x`

Basic Chisel Constructs

Chisel Wire Operators:

```
// Allocate a as wire of type UInt()
val x = Wire(UInt())
x := y // Connect wire y to wire x
```

When executes blocks conditionally by `Bool`, and is equivalent to Verilog `if`

```
when(condition1) {
  // run if condition1 true and skip rest
}.elsewhen(condition2) {
  // run if condition2 true and skip rest
}.otherwise {
  // run if none of the above ran
}
```

Switch executes blocks conditionally by data

```
switch(x) {
  is(value1) {
    // run if x === value1
  }
  is(value2) {
    // run if x === value2
  }
}
```

Enum generates value literals for enumerations

```
val s1:s2:...::sn::Nil
  = Enum(nodeType:UInt, n:Int)
s1, s2, ..., sn will be created as nodeType literals
with distinct values
nodeType type of s1, s2, ..., sn
n element count
```

Math Helpers:
`log2Ceil(in: Int): Int` \log_2 (in) rounded up
`log2Floor(in: Int): Int` \log_2 (in) rounded down
`isPow2(in: Int): Boolean` True if in is a power of 2

Hardware Generation

Functions provide block abstractions for code. Scala functions that instantiate or return Chisel types are code generators.

Also: Scala's `if` and `for` can be used to control hardware generation and are equivalent to Verilog `generate if/for`

```
val number = Reg(if(can_be_negative) SInt()
                  else UInt())
// will create a Register of type SInt or UInt depending on
// the value of a Scala variable
```

Aggregate Types

Bundle contains Data types indexed by name

Defining: subclass `Bundle`, define components:

```
class MyBundle extends Bundle {
  val a = Bool()
  val b = UInt(32.W)
}
```

Constructor: instantiate `Bundle` subclass:

```
val my_bundle = new MyBundle()
// inline defining: define a Bundle type:
val my_bundle = new Bundle {
  val a = Bool()
  val b = UInt(32.W)
}
```

Using: access elements through dot notation:

```
val bundleVal = my_bundle.a
my_bundle.a := true.B
```

Vec is an indexable vector of Data types

```
val myVec = Vec(elts:Iterable[Data])
elts initial element Data (vector depth inferred)
val myVec = Vec.fill(n:Int) {gen:Data}
n vector depth (elements)
gen initial element Data, called once per element
Using: access elements by dynamic or static indexing:
readVal := myVec(ind: UInt / idx: Int)
myVec(ind: UInt / idx: Int) := writeVal
Functions: (T is the Vec element's type)
.forall(p:T=>Bool): Bool AND-reduce p on all elts
.exists(p:T=>Bool): Bool OR-reduce p on all elts
.contains(x:T): Bool True if this contains x
.count(p:T=>Bool): UInt count elts where p is True
```

Basic Data Types

Constructors:

`Bool()` type, boolean value
`true.B` or `false.B` literal values
`UInt(32.W)` type 32-bit unsigned
`UInt()` type, width inferred
`77.U` or `"head".U` unsigned literals
`1.U(16.W)` literal with forced width
`SInt()` or `ISInt(64.W)` like `UInt`
`-3.S` signed literals
`3.S(2.W)` signed 2-bits wide value -1
Bits, UInt, SInt Casts: reinterpret cast except for:
`UInt -> SInt` Zero-extend to `SInt`

State Elements

Registers retain state until updated

```
val my_reg = Reg(UInt(32.W))
// Flavors
RegInit(7.U(32.W)) reg with initial value 7
RegNext(next_val) update each clock, no init
RegNext(next, init) update, with init
RegEnable(next, enable) update, with enable gate
Updating: assign to latch new value on next clock:
my_reg := next_val
```

Read-Write Memory provide addressable memories

```
val my_mem = Mem(n:Int, out:Data)
out memory element type
n memory depth (elements)
Using: access elements by indexing:
val readVal = my_mem(addr:UInt/Int)
for synchronous read: assign output to Reg
my_mem(addr:UInt/Int) := y
```

Modules

Defining: subclass `Module` with elements, code:

```
class Accum(width:Int) extends Module {
  val io = IO(new Bundle {
    val in = Input(UInt(width.W))
    val out = Output(UInt(width.W))
  })
  val sum = Reg(UInt())
  sum := sum + io.in
  io.out := sum
}
```

Usage: access elements using dot notation:
(code inside a `Module` is always running)

```
val my_module = Module(new Accum(32))
my_module.io.in := some_data
val sum := my_module.io.out
```

Operators:

Chisel	Explanation	Width
<code>!x</code>	Logical NOT	1
<code>x && y</code>	Logical AND	1
<code>x y</code>	Logical OR	1
<code>x(n)</code>	Extract bit, 0 is LSB	1
<code>x(n, m)</code>	Extract bitfield	$n - m + 1$
<code>x << y</code>	Dynamic left shift	$w(x) + \maxVal(y)$
<code>x >> y</code>	Dynamic right shift	$w(x) - \minVal(y)$
<code>x << n</code>	Static left shift	$w(x) + n$
<code>x >> n</code>	Static right shift	$w(x) - n$
<code>Fill(n, x)</code>	Replicate x, n times	$n * w(x)$
<code>Cat(x, y)</code>	Concatenate bits	$w(x) + w(y)$
<code>Mux(c, x, y)</code>	If c, then x; else y	$\max(w(x), w(y))$
<code>~x</code>	Bitwise NOT	$w(x)$
<code>x & y</code>	Bitwise AND	$\max(w(x), w(y))$
<code>x y</code>	Bitwise OR	$\max(w(x), w(y))$
<code>x ^ y</code>	Bitwise XOR	$\max(w(x), w(y))$
<code>x === y</code>	Equality (triple equals)	1
<code>x != y</code>	Inequality	1
<code>x + y</code>	Addition	$\max(w(x), w(y))$
<code>x +% y</code>	Addition	$\max(w(x), w(y))$
<code>x +k y</code>	Addition	$\max(w(x), w(y)) + 1$
<code>x - y</code>	Subtraction	$\max(w(x), w(y))$
<code>x -% y</code>	Subtraction	$\max(w(x), w(y))$
<code>x -k y</code>	Subtraction	$\max(w(x), w(y)) + 1$
<code>x * y</code>	Multiplication	$w(x) + w(y)$
<code>x / y</code>	Division	$w(x)$
<code>x % y</code>	Modulus	$\max(w(x), w(y)) - 1$
<code>x > y</code>	Greater than	1
<code>x >= y</code>	Greater than or equal	1
<code>x < y</code>	Less than	1
<code>x <= y</code>	Less than or equal	1
<code>x >> y</code>	Arithmetic right shift	$w(x) - \minVal(y)$
<code>x >> n</code>	Arithmetic right shift	$w(x) - n$

UInt bit-reduction methods:

Chisel	Explanation	Width
<code>x.andR</code>	AND-reduce	1
<code>x.orR</code>	OR-reduce	1
<code>x.xorR</code>	XOR-reduce	1

As an example to apply the `andR` method to an `SInt` use `x.asUInt.andR`

gen Chisel Data to wrap ready-valid protocol around

Interface:

```
(in) .ready ready Bool
(out) .valid valid Bool
(out) .bits data
```

ValidIO is a `Bundle` with a valid interface

Constructor:

`Valid(gen:Data)`
gen Chisel Data to wrap valid protocol around

Interface:

```
(out) .valid valid Bool
(out) .bits data
```

Queue is a `Module` providing a hardware queue

Constructor:

```
Queue(enq:DecoupledIO, entries:Int)
enq DecoupledIO source for the queue
entries size of queue
```

Interface:

```
.io.enq DecoupledIO source (flipped)
.io.deq DecoupledIO sink
.io.count UInt count of elements in the queue
```

Pipe is a `Module` delaying input data

Constructor:

`Pipe(enqValid:Bool, enqBits:Data, [latency:Int])`

`Pipe(enqValidIO, [latency:Int])`
enqValid input data, valid component
enqBits input data, data component
enq input data as `ValidIO`
latency (optional, default 1) cycles to delay data by

Interface:

```
.io.enq ValidIO source (flipped)
.io.deq ValidIO sink
```

Arbiters are `Modules` connecting multiple producers

to one consumer

Arbiter prioritizes lower producers

RRArbiter runs in round-robin order

Constructor:

`Arbiter(gen:Data, n:Int)`

gen data type

n number of producers

Interface:

```
.io.in Vec of DecoupledIO inputs (flipped)
.io.out DecoupledIO output
.io.chosen UInt input index on .io.out,
does not imply output is valid
```